
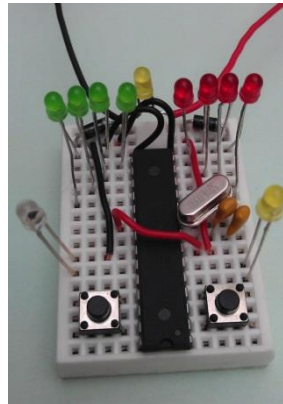


# Microcontroller build steps

Engineer's training guide V1.1

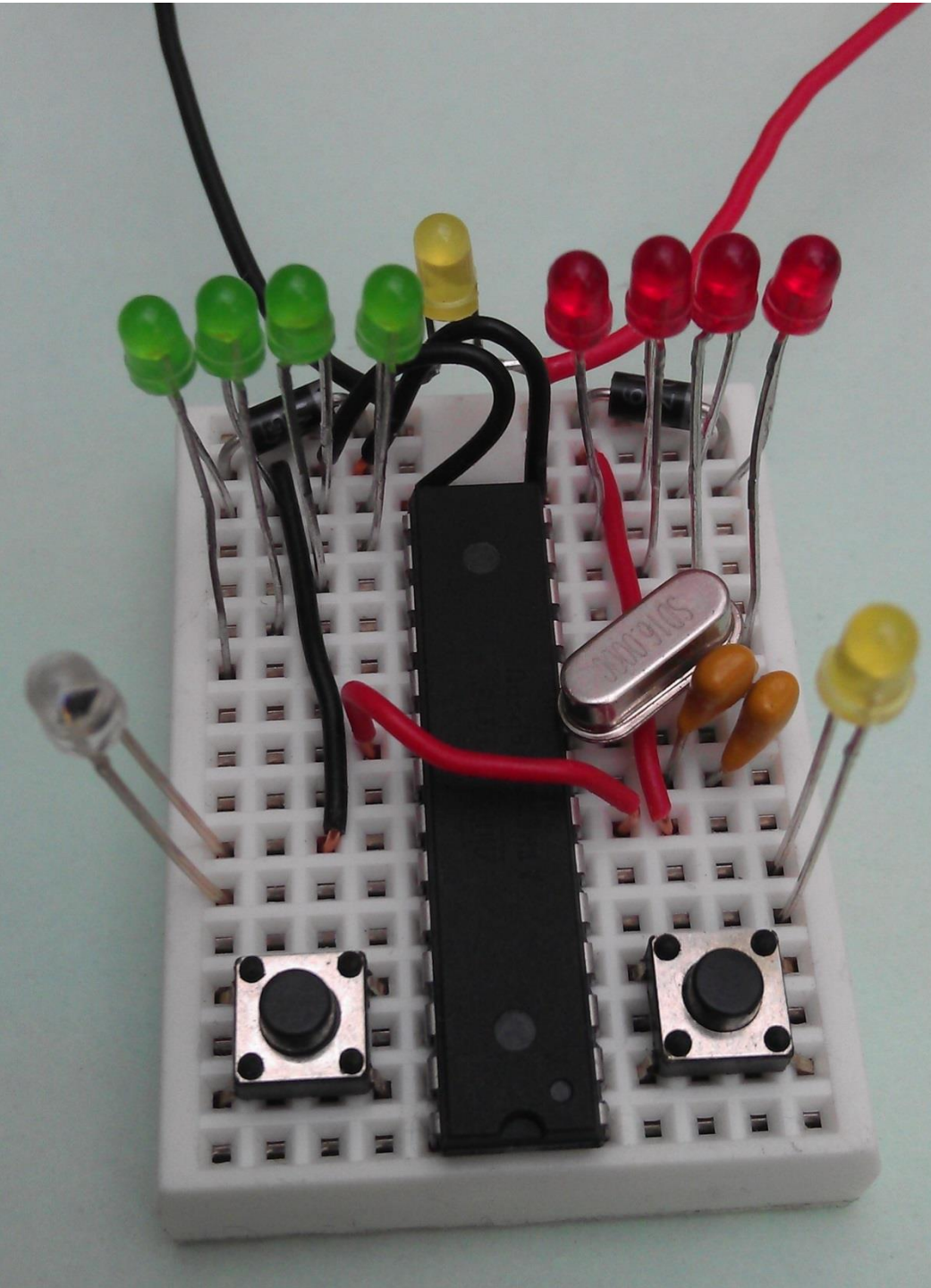





Atmel



Noble Touch

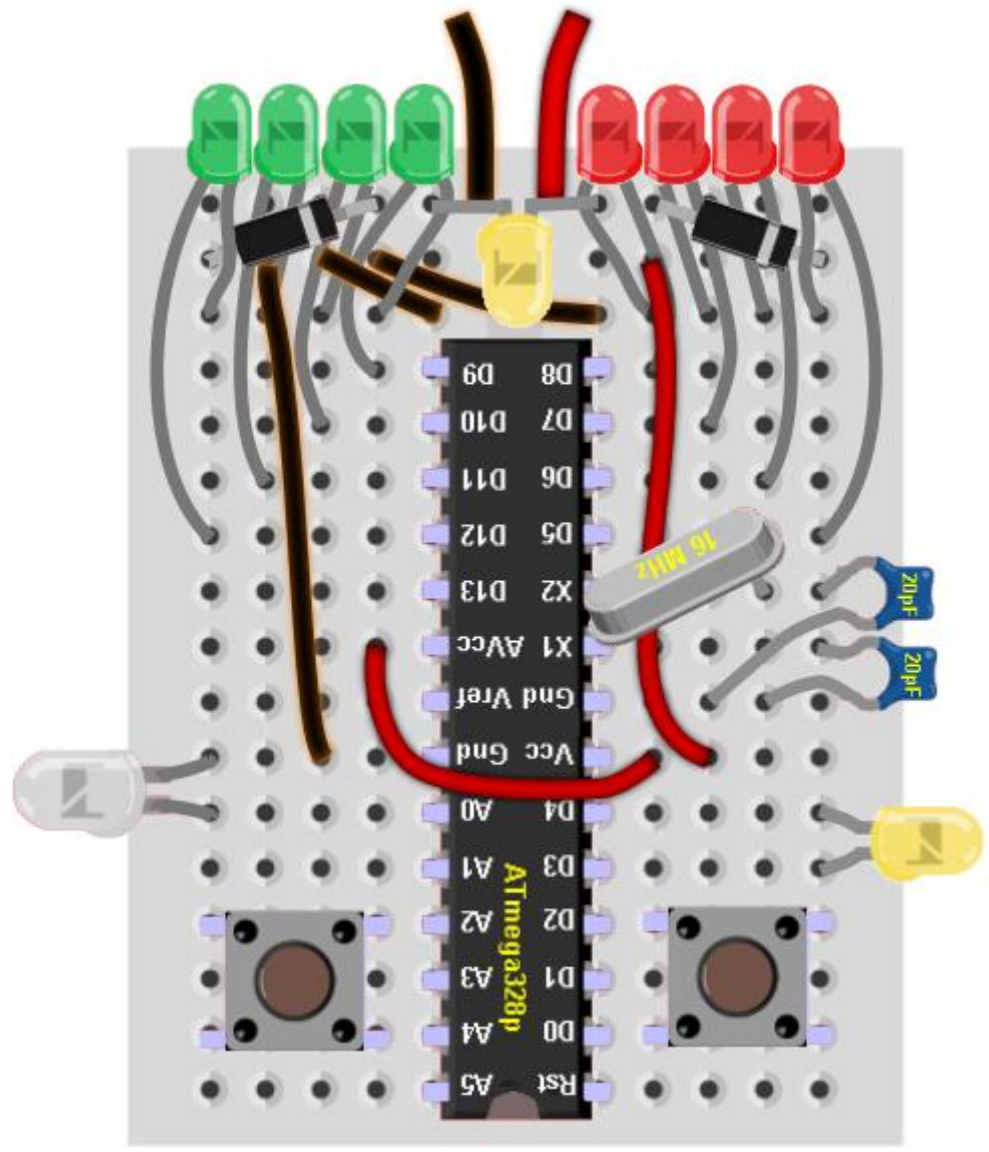

# Convention used

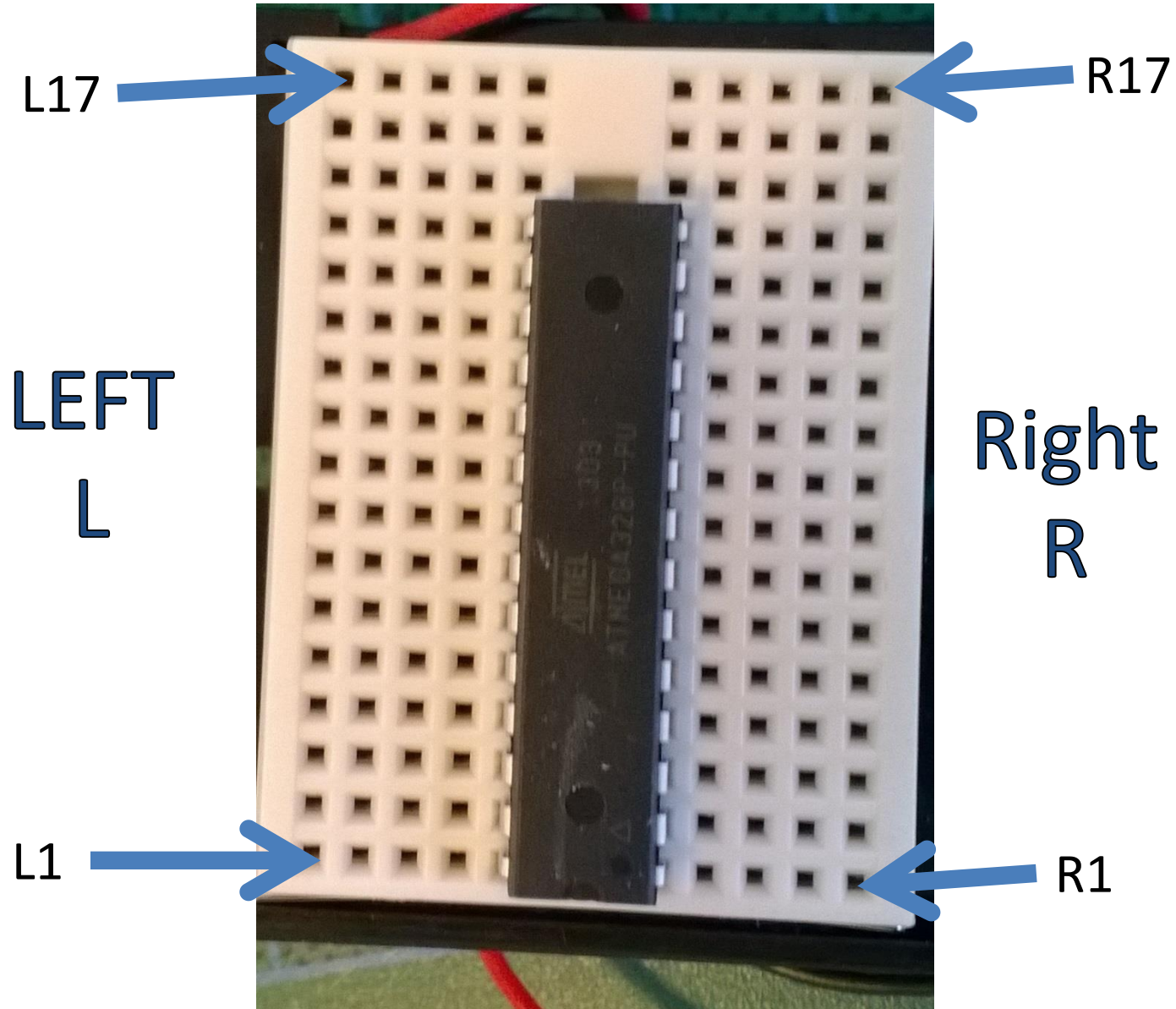

## Red Jump wires

RED        R7 – L9

RED        R7 – R16

Red    =    +ve Vcc

Black =    -ve GND



## Black Jump wires

BLACK L7 – L16

BLACK L15 – L16


BLACK R15 – L16

Red = +ve Vcc

Black = -ve GND



# Momentary Switches

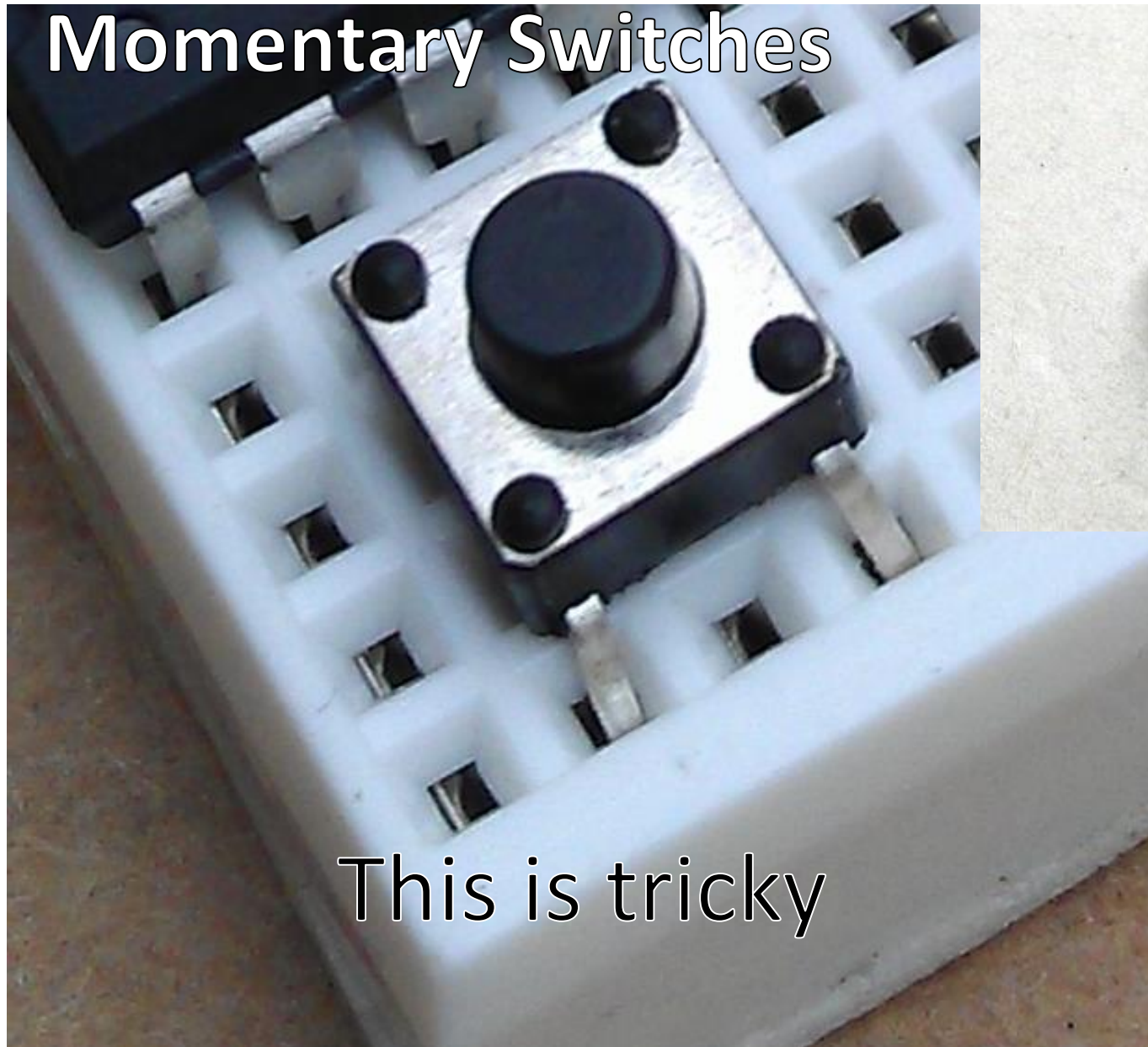

This is tricky



Switch 1

R2 – R4


Switch 2

L2 – L4

## Diodes - Note the stripe

Diode1 L16 – L17 (White stripe)

Diode2 R17 – R16 (White stripe)

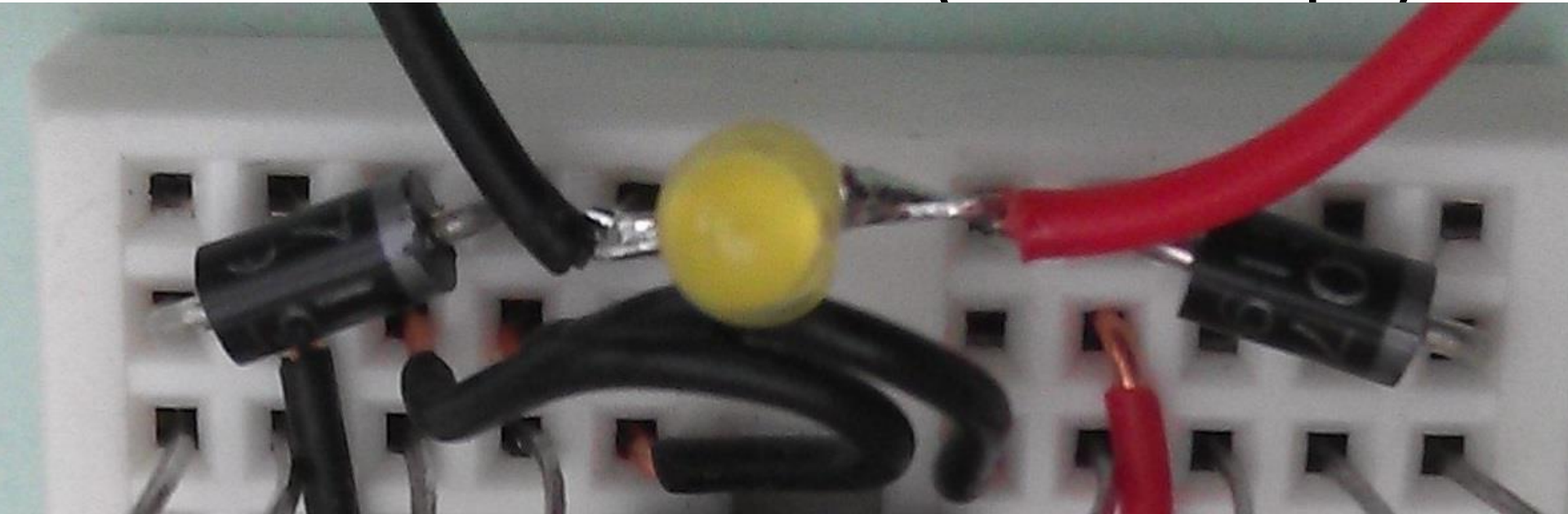


Fresh alkaline AAA = 2 Diodes

Rechargeable = 1 or zero Diodes



# 16MHz Crystal Oscillator

XTAL R9 – R10

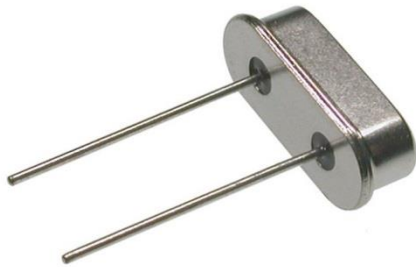

# Capacitors

CAP1      R8 – R9

CAP2      R8 – R10



## RED LEDs


NOTE: All SHORT LEGS – 15R

LED R14 – R15

LED R13 – R15

LED R12 – R15

LED R11 – R15

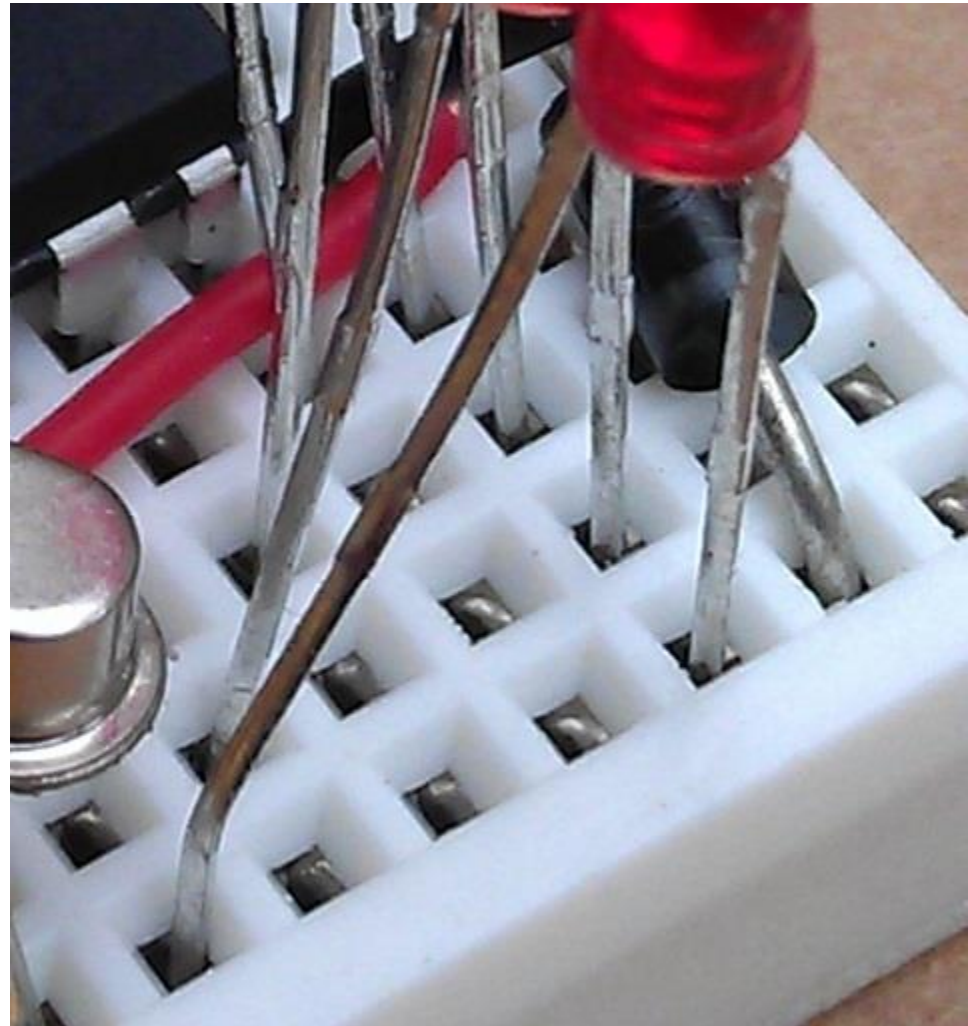

## Green LEDs


NOTE: All SHORT LEGS – L15

LED L14 – L15

LED L13 – L15


LED L12 – L15

LED L11 – L15

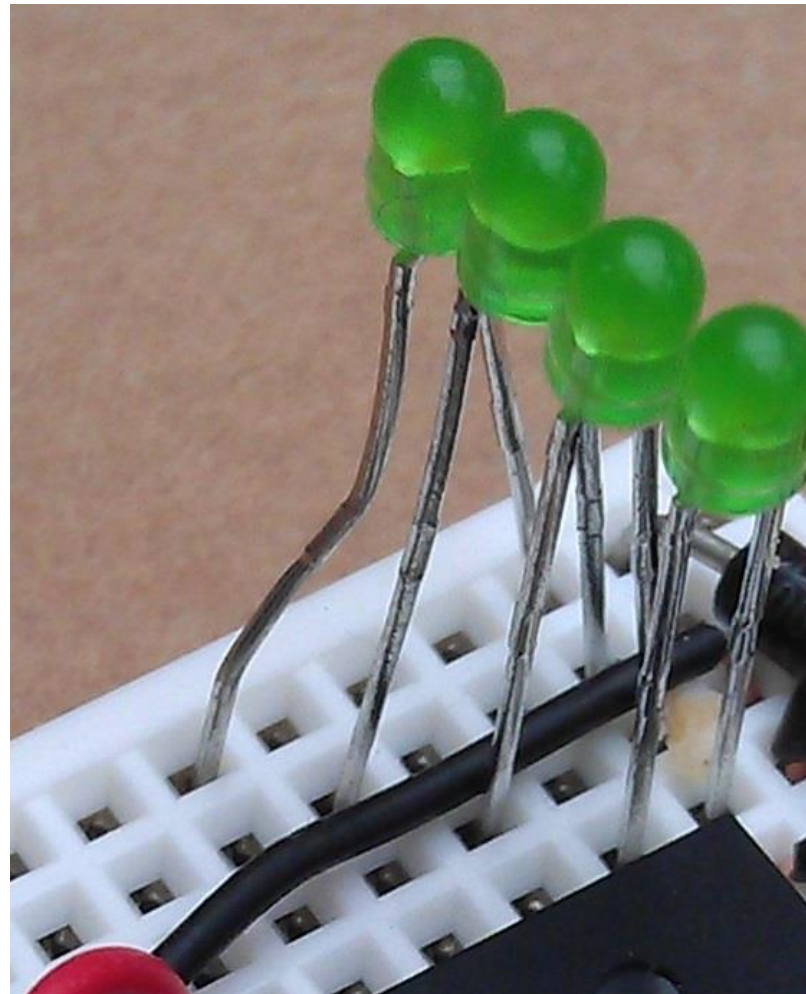


# Photo Transistor

L6 – L7 (Short leg)

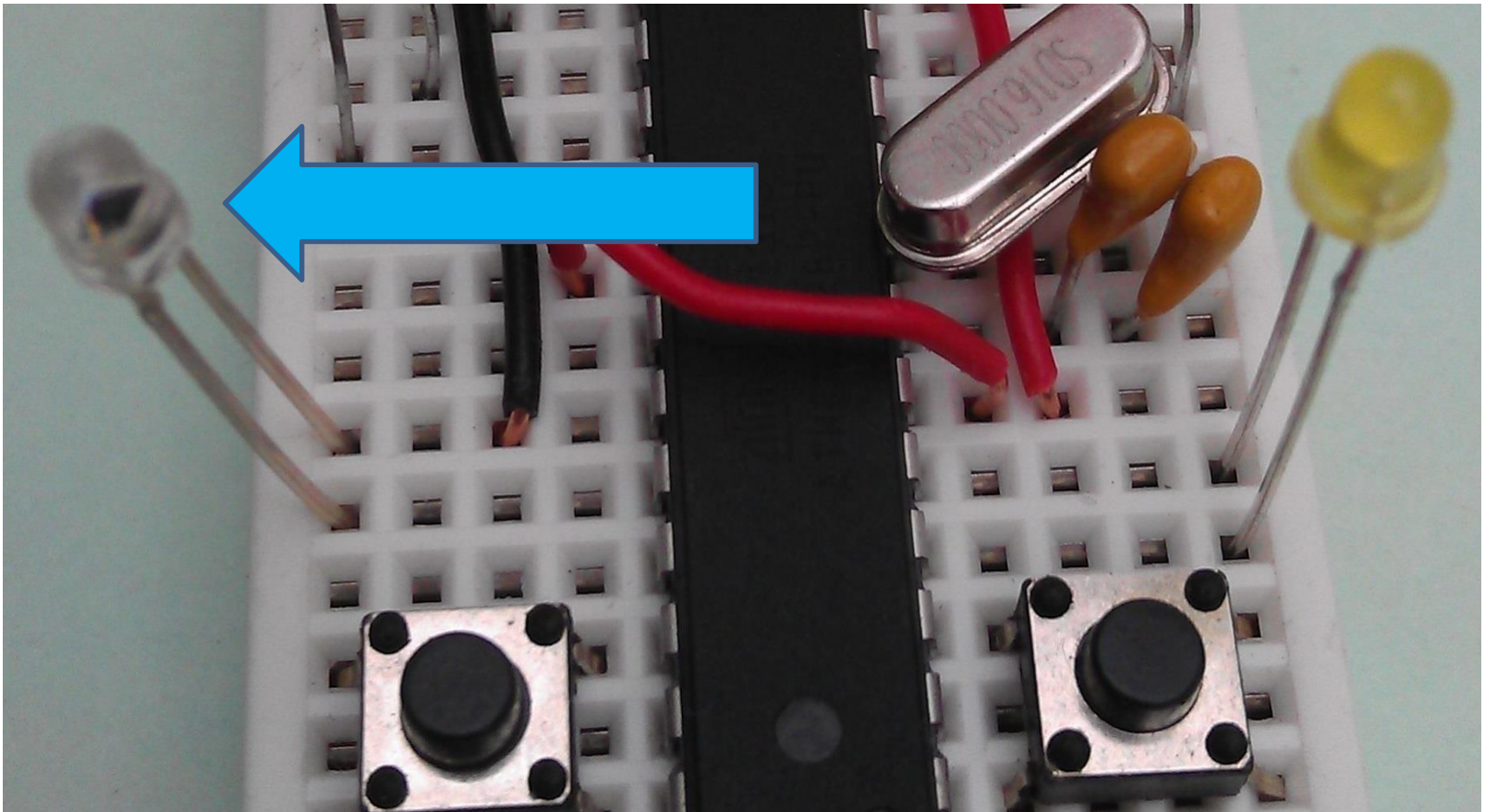

# Yellow LED

LED R5 – R6 (Short leg)

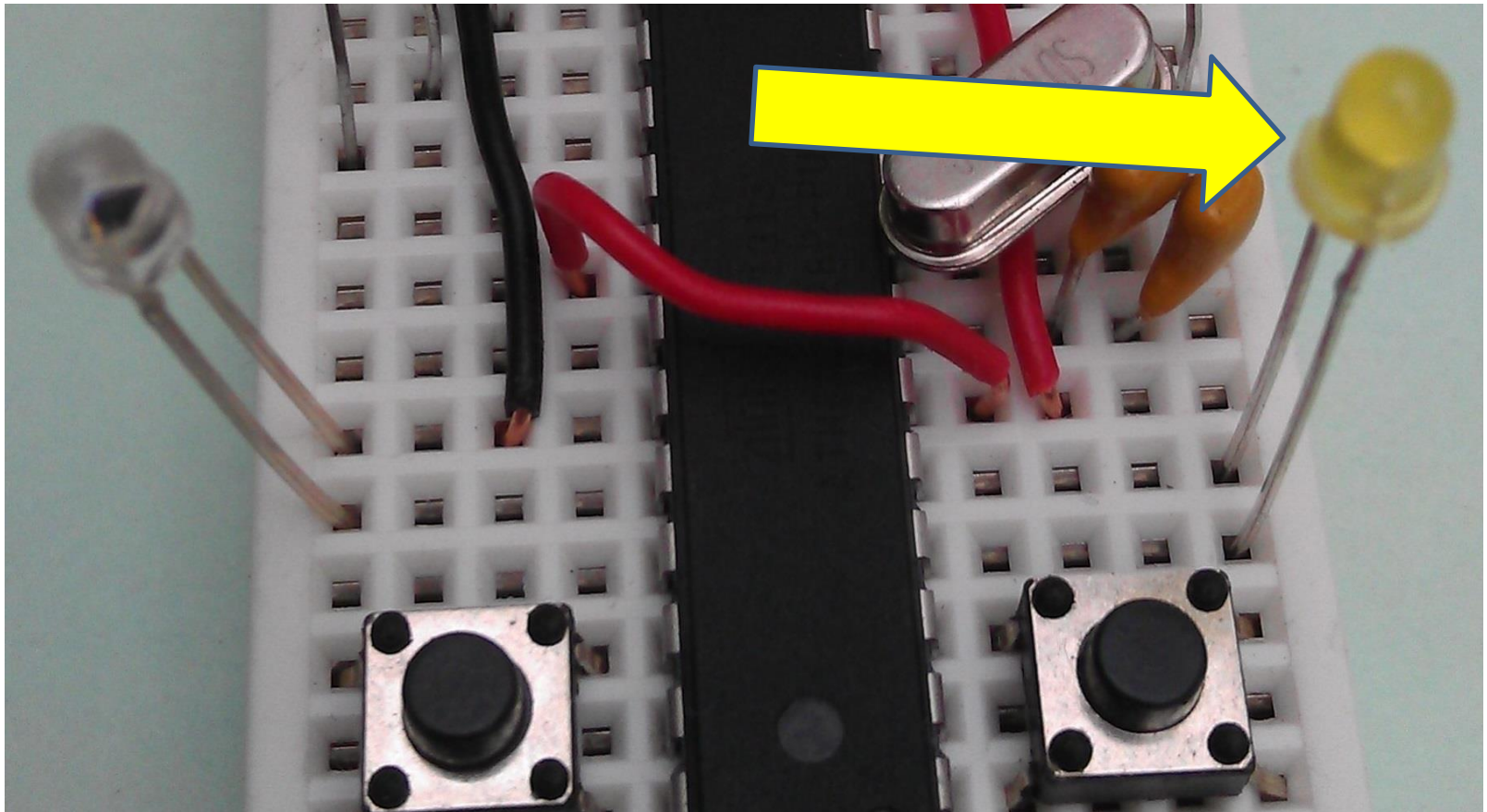


# Power UP

Connect the battery box

Red wire – R17

Black wire – L17

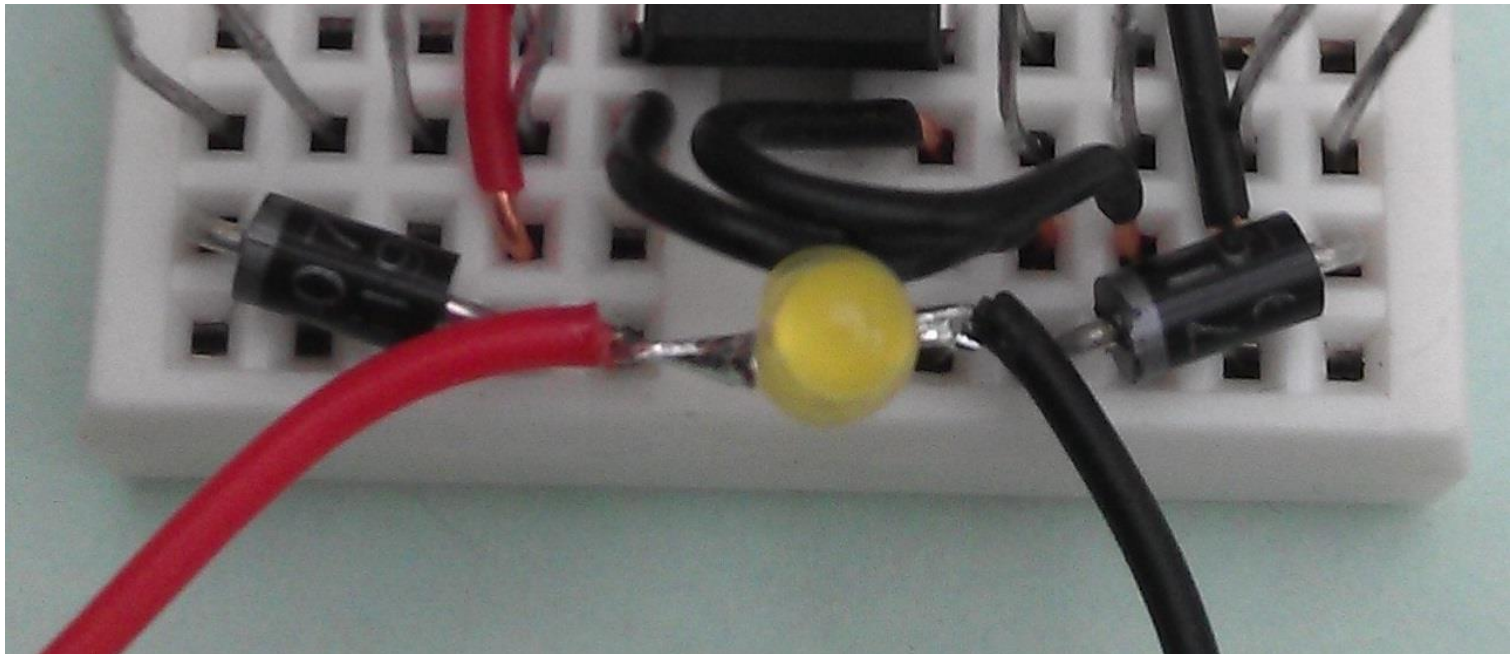

# Modes

1) Random Flashing lights

2) LED Count 1

3) LED Count 2

4) LED Click count

- Left button adds one to the click count

5) Light level with PWM

- Left button used to calibrate level

6) Temperature mode

- Left button used to calibrate level



# Feedback

## Feedback from a recent test build

1. The wires are quite stiff. Grip the plastic sheath of the wire and push from there. Because the wires are hard to push in there is a temptation to push the other end of the wire. Do not do this as the cut end of the wire is sharp and it hurts!
2. The diodes are extra hard to push in, and need a good push at both ends and then check they are both the right way round.
3. The switches are a bit fiddly but if you apply a thumbnail to each side and press down then they go in quite easily.
4. Components, like LEDs, with one short led and one long leg must have the short led towards the diodes end of the board.